

## Experiment -12

Title: Implementation of T – Flip Flop circuit in Behavioural Modelling.


Objective: To understand the working of the T – Flip Flop circuit.

Theory: A T Flip-Flop is like a JK Flip-Flop. These are basically a single input version of JK Flip-Flops. This is modified form of JK Flip-Flop is obtained by connecting both inputs J and K together. It has only one input along with the clock input.

Truth Table:

T	Q	Q(t+1)
0	0	0
1	0	1
0	1	1
1	1	0

Circuit Diagram:

 

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity T_FLIP_FLOP is
  Port(T: In STD_LOGIC;
        CLK: In STD_LOGIC;
        Q: Out STD_LOGIC);
end T_FLIP_FLOP;
```

architecture Behavioral of T\_FLIP\_FLOP is

begin

process(CLK, T) is

variable MEM: STD\_LOGIC := '0';

begin

if(CLK = '1' and CLK'EVENT)then

if(T = '1')then

MEM := NOT(MEM);

end if;


end if;

Q <= MEM;


end process;

end Behavioral;


### Entity Diagram:

 

### RTL Schematic:

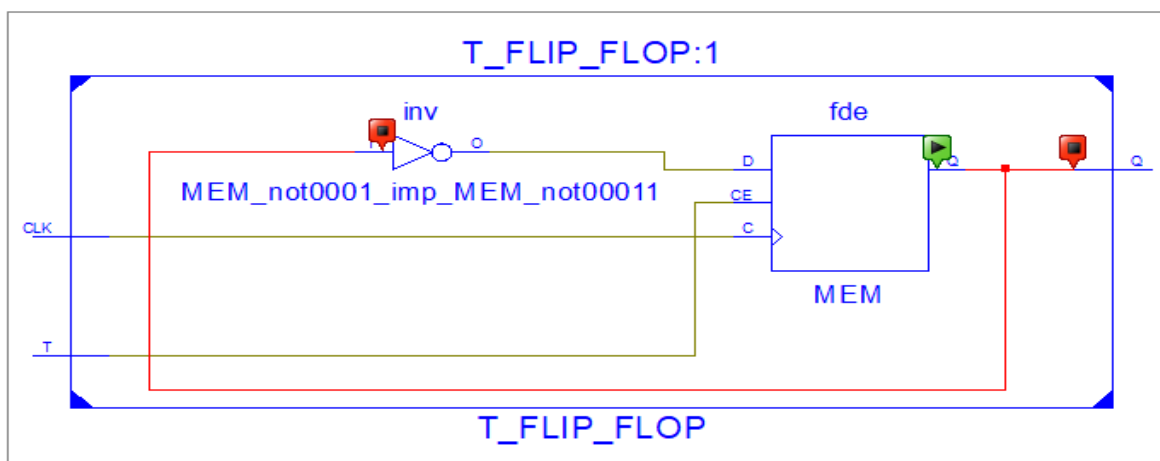

## Output:

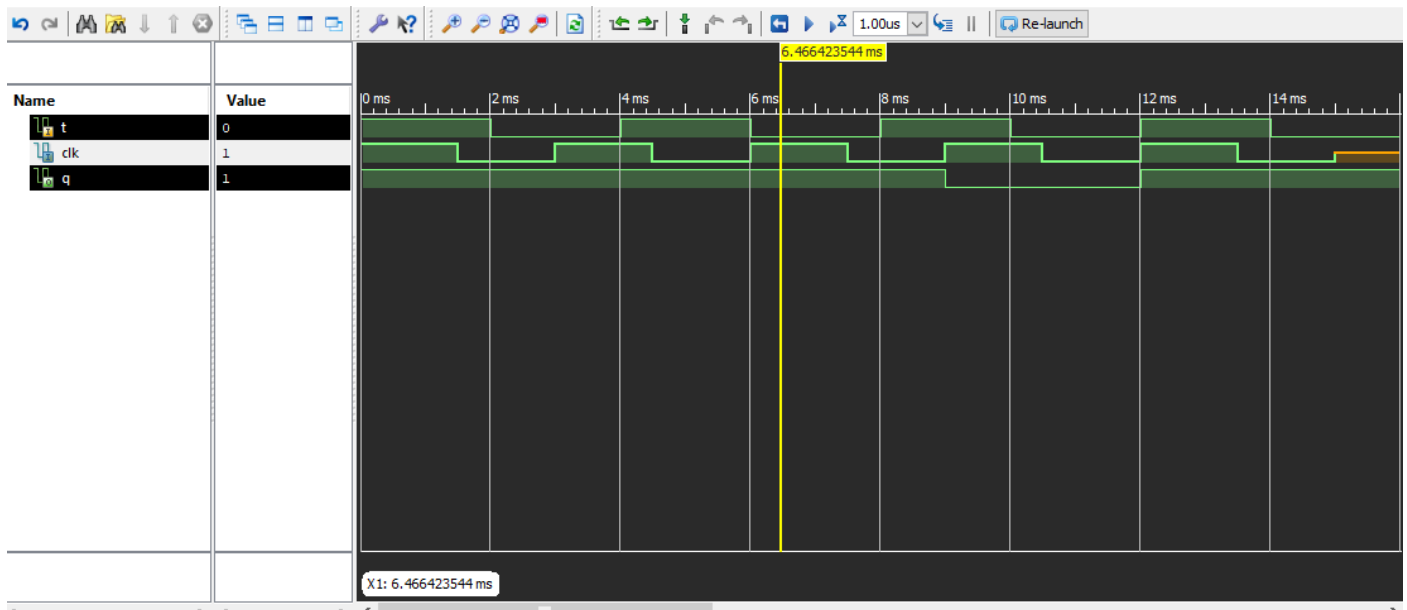

Result: We have implemented a T Flip-Flop circuit in Behavioural modelling using case statement , and the RTL Schematic and the Simulation Waveform are shown above.

## Conclusion:

In this experiment , we learnt about case statement in VHDL and used it to implement a T Flip-Flop circuit.