

Experiment-7

Title: Implementation of a 3-8 Decoder.


Objective: To implement a 3-8 decoder in behavioural modelling.

Theory:

The combinational circuit that changes the binary information into 2^N output lines is known as **Decoders**. The binary information is passed in the form of N input lines. The output lines define the 2^N -bit code for the binary information. In simple words, the **Decoder** performs the reverse operation of the **Encoder**. At a time, only one input line is activated for simplicity. The produced 2^N -bit output code is equivalent to the binary information.

The 3 to 8 line decoder is also known as **Binary to Octal Decoder**. In a 3 to 8 line decoder, there is a total of eight outputs, i.e., $Y_0, Y_1, Y_2, Y_3, Y_4, Y_5, Y_6$, and Y_7 and three outputs, i.e., A_0, A_1 , and A_2 . This circuit has an enable input 'E'. Just like 2 to 4 line decoders, when enable 'E' is set to 1, one of these four outputs will be 1. The block diagram and the truth table of the 3 to 8 line encoder are given below.

Block Diagram:

 

Truth Table:

Enable	INPUTS			Outputs							
E	A ₂	A ₁	A ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

The logical expression of the term Y₀, Y₁, Y₂, Y₃, Y₄, Y₅, Y₆, and Y₇ is as follows:

$$Y_0 = A_0' \cdot A_1' \cdot A_2'$$

$$Y_1 = A_0 \cdot A_1' \cdot A_2'$$

$$Y_2 = A_0' \cdot A_1 \cdot A_2'$$

$$Y_3 = A_0 \cdot A_1 \cdot A_2'$$

$$Y_4 = A_0' \cdot A_1' \cdot A_2$$

$$Y_5 = A_0 \cdot A_1' \cdot A_2$$

$$Y_6 = A_0' \cdot A_1 \cdot A_2$$

$$Y_7 = A_0 \cdot A_1 \cdot A_2$$

Code:

```
library IEEE;


use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_8 is
    Port(x2: in std_logic;
          x1: in std_logic;
          x0: in std_logic;
          y: out std_logic_vector(0 to 7));
end Decoder_3_8;


architecture Decoder of Decoder_3_8 is
begin
    process(x2)
        variable x: std_logic_vector(0 to 2);
        begin
            x:= x2&x1&x0;

            case x is
                when "000" => y <= "00000001";
                when "001" => y <= "00000010";
                when "010" => y <= "00000100";
                when "011" => y <= "00001000";
                when "100" => y <= "00010000";
                when "101" => y <= "00100000";
                when "110" => y <= "01000000";
                when "111" => y <= "10000000";
                when others => y <= "00000000";
            end case;
        end process;
    end Decoder;
```


Entity Diagram:

 

RTL Schematic:

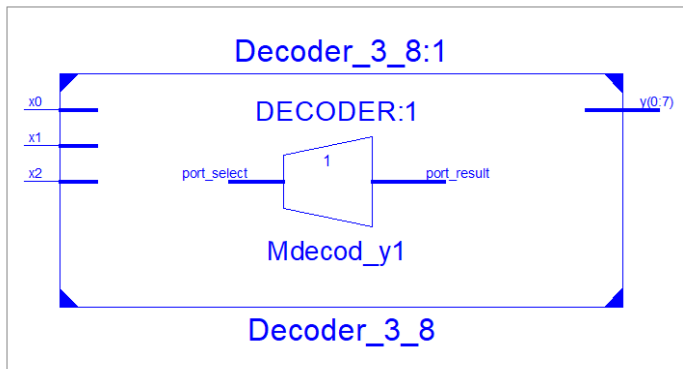

Output:

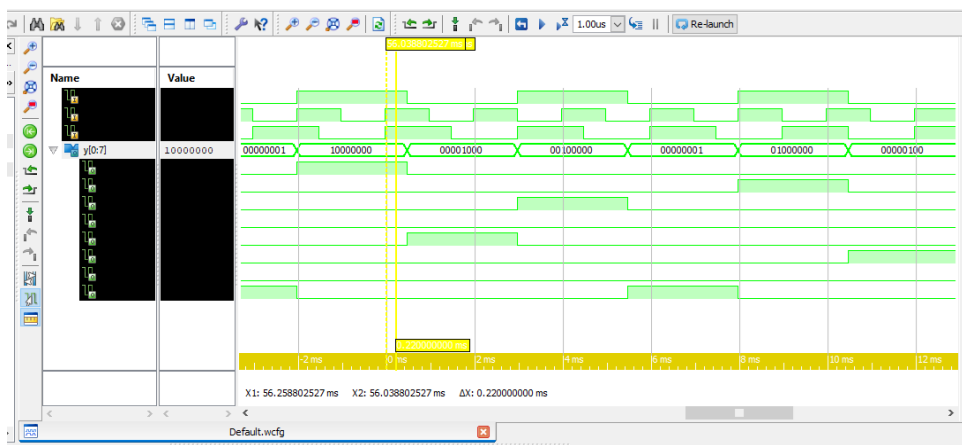

Result:

We have implemented a 3-8 Decoder in VHDL using Behavioural modelling, and the Entity Diagram, RTL schematic and the output are shown above.

Conclusion:

In this experiment, we learnt about behavioural modelling in VHDL and used it to implement a 3-8 Decoder.