

Experiment-3

Question: Verify the Truth table of all the basic logic gates using VHDL.

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity BASIC_GATES is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        AND_OUT : out STD_LOGIC;
        OR_OUT : out STD_LOGIC;
        NOT_OUT : out STD_LOGIC;
        NAND_OUT : out STD_LOGIC;
        NOR_OUT : out STD_LOGIC;
        XOR_OUT : out STD_LOGIC;
        XNOR_OUT: out STD_LOGIC);
end BASIC_GATES;

architecture Behavioral of BASIC_GATES is

begin

  process(A,B)
  begin
    if((A = '1') AND (B = '1')) THEN
      AND_OUT <= '1';
    else
      AND_OUT <= '0';
    end if;
    if((A = '0') AND (B = '0')) THEN
      OR_OUT <= '0';
    else
      OR_OUT <= '1';
    end if;
    if((A = '0') AND (B = '0')) THEN
      NOR_OUT<= '1';
    else
      NOR_OUT <= '0';
    end if;

    if(A = '1') THEN
```


```

        NOT_OUT <= '0';
    else
        NOT_OUT <= '1';
    end if;
    if((A = '1') AND (B = '1')) THEN
        NAND_OUT <= '0';
    else
        NAND_OUT <= '1';
    end if;
    if((A /= B)) THEN
        XOR_OUT <= '1';
    else
        XOR_OUT <= '0';
    end if;


    if((A /= B)) THEN
        XNOR_OUT <= '0';
    else
        XNOR_OUT <= '1';
    end if;
end process;
end Behavioral;

```

Entity Diagram

 

Detailed Entity Diagram

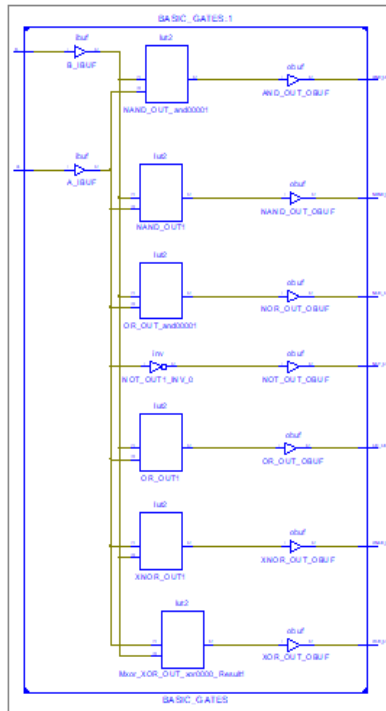

Output:

