

## Experiment-8

**Title:** Implementation of a 4:1 MUX from 2:1 MUX.

**Objective:** To implement a 4:1 MUX using 2:1 MUX in VHDL using structural modelling.

**Theory:**


### **Multiplexer:**

In electronics, a **multiplexer** (or **mux**; spelled sometimes as **multiplexor**), also known as a **data selector**, is a device that selects between several analog or digital input signals and forwards the selected input to a single output line. The selection is directed by a separate set of digital inputs known as select lines. A multiplexer of  $2^n$  inputs has  $n$  select lines, which are used to select which input line to send to the output.

### **2:1 Multiplexer:**

In a 2:1 multiplexer, there are only two inputs, i.e.,  $A_0$  and  $A_1$ , 1 selection line, i.e.,  $S_0$  and single outputs, i.e.,  $Y$ . On the basis of the combination of inputs which are present at the selection line  $S_0$ , one of these 2 inputs will be connected to the output. The block diagram and the truth table of the  $2 \times 1$  multiplexer are given below.

### **Block Diagram:**

 


## Truth Table:

INPUTS	Output
$S_0$	Y
0	$A_0$
1	$A_1$

The logical expression of the term Y is as follows:

$$Y = S_0' \cdot A_0 + S_0 \cdot A_1$$

 
Logical circuit of the above expression is given below:



## 4×1 Multiplexer:

In the 4×1 multiplexer, there are a total of four inputs, i.e.,  $A_0$ ,  $A_1$ ,  $A_2$ , and  $A_3$ , 2 selection lines, i.e.,  $S_0$  and  $S_1$  and single output, i.e.,  $Y$ . On the basis of the combination of inputs that are present at the selection lines  $S_0$  and  $S_1$ , one of these 4 inputs are connected to the output. The block diagram and the truth table of the 4×1 multiplexer are given below.

## Block Diagram:

 


### Truth Table:

INPUTS		Output
$S_1$	$S_0$	$Y$
0	0	$A_0$
0	1	$A_1$
1	0	$A_2$
1	1	$A_3$

The logical expression of the term  $Y$  is as follows:

$$Y = S_1' S_0' A_0 + S_1' S_0 A_1 + S_1 S_0' A_2 + S_1 S_0 A_3$$

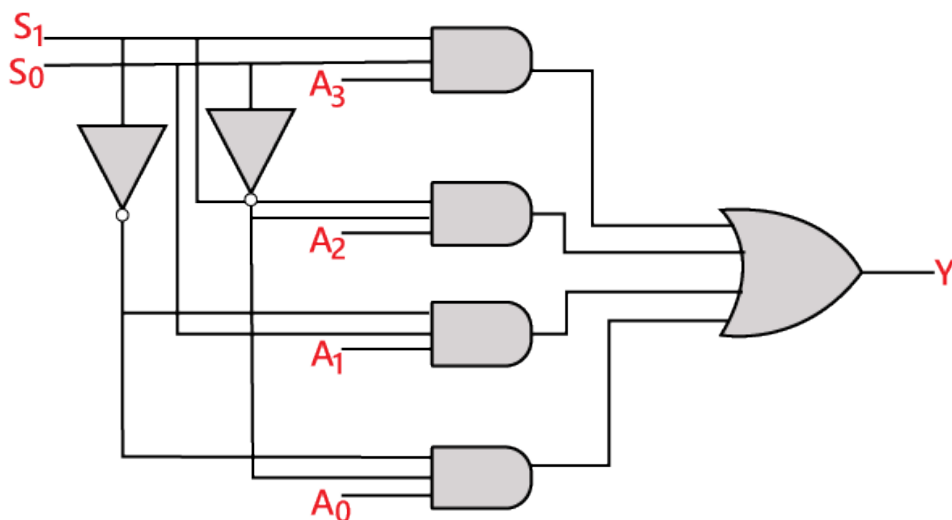Logical circuit of the above expression is given below:



## **Code:**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity MUX\_4\_1 is

Port ( D0 : in STD\_LOGIC;

D1 : in STD\_LOGIC;

D2 : in STD\_LOGIC;

D3 : in STD\_LOGIC;

S0 : in STD\_LOGIC;

S1 : in STD\_LOGIC;

Y : out STD\_LOGIC);

end MUX\_4\_1;

architecture Structural of MUX\_4\_1 is

Component MUX\_2\_1 is

Port(P, Q, R : in STD\_LOGIC;

O : out STD\_LOGIC);

end Component;

Signal P1,P2 : STD\_LOGIC;

begin


N1 : MUX\_2\_1 PORT MAP(D0,D1,S1,P1);

N2 : MUX\_2\_1 PORT MAP(D2,D3,S1,P2);


N3 : MUX\_2\_1 PORT MAP(P1,P2,S0,Y);

end structural;

## Entity Diagram:

 

## RTL Schematic:

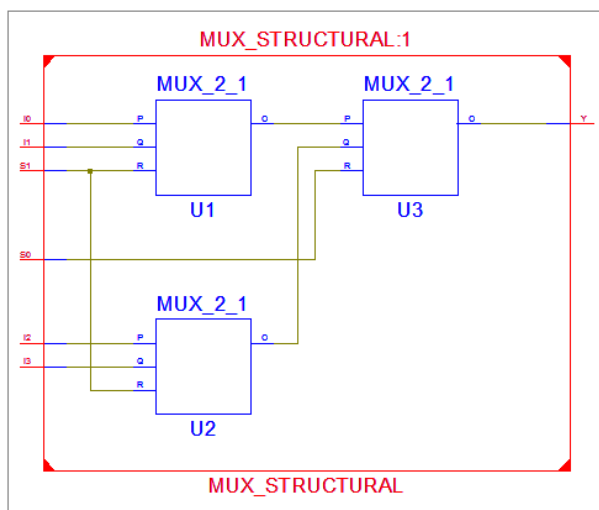

## Result:

We have implemented a 4:1 Multiplexer from 2:1 multiplexers in VHDL structural modelling, and the Entity Diagram and the RTL schematic are shown above.

## Conclusion:

In this experiment, we learnt about structural modelling in VHDL and used it to implement a 4:1 Multiplexer.